



**ZEAL EDUCATION SOCIETY'S  
ZEAL COLLEGE OF ENGINEERING AND RESEARCH  
NARHE | PUNE -41 | INDIA**



Record No.: ZCOER-ACAD/R/16M

Revision: 00

Date: 01/04/2021

**Unit Wise Question Bank**

**Department: FY BTech**

**Semester: I**

**Academic Year: 2024-25**

**Class: FY COMP, IT, AIDS, AIML**

**Div.: A, B, C**

**Date: 26.12.2024**

**Course: Basic Electrical And Electronics Engineering**

Unit No. - name	Q. No .	Question	Marks	CO	Blooms Level														
Unit 6: Digital Electronics Fundamenta 1	1.	Write the Symbol, Truth Table and Output Expression for following gates. 1) OR 2) NAND	5	6	1														
	<div><div><div><div><div></div><div>A</div></div><div><div></div><div>B</div></div></div><div><div></div><div>C</div></div></div></div> <div><table><tr><th>A</th><th>B</th><th>C</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table><div><div>Y = A + B</div></div></div> <div>1 Marks</div> <div>1 Marks</div> <div>½ Marks</div>					A	B	C	0	0	0	0	1	1	1	0	1	1	1
A	B	C																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

**Course Faculty**

**Prof. Karuna Mahajan**




**ZEAL EDUCATION SOCIETY'S  
ZEAL COLLEGE OF ENGINEERING AND RESEARCH  
NARHE | PUNE -41 | INDIA**



Record No.: **ZCOER-ACAD/R/16M**

Revision: **00**

Date: **01/04/2021**

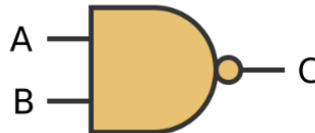

1 Marks

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

1 Marks

$$Y = \underline{AB}$$

½ Marks

2.

Write the Symbol, Truth table and Output Expression for following gates.


- 1) NOR
- 2) AND

5

6

2

### NOR GATE

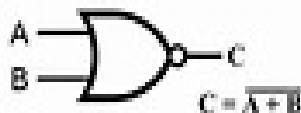

TRUTH TABLE		
INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

1 mark -symbol

1 mark -truth table

½ mark-symbol

Course Faculty

Prof. Karuna Mahajan




**ZEAL EDUCATION SOCIETY'S**  
**ZEAL COLLEGE OF ENGINEERING AND RESEARCH**  
**NARHE | PUNE -41 | INDIA**



Record No.: **ZCOER-ACAD/R/16M**

Revision: **00**

Date: **01/04/2021**

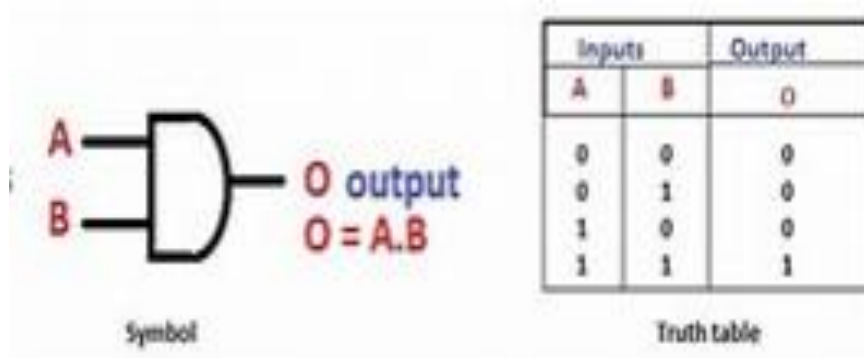

AND GATE

1 mark -symbol

1 mark -truth table

½ mark-symbol

3.


Write the Symbol, Truth table and Output Expression for following gates.

- 1) Ex-OR
- 2) NOT

5

6

2

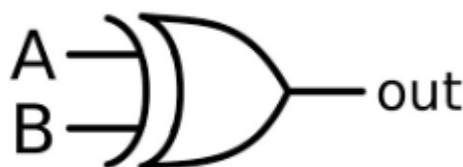

A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0

EX-OR Gate  $Y = A \oplus B$

1 mark -symbol

1 mark -truth table

½ mark-symbol



**ZEAL EDUCATION SOCIETY'S  
ZEAL COLLEGE OF ENGINEERING AND RESEARCH  
NARHE | PUNE -41 | INDIA**




Record No.: ZCOER-ACAD/R/16M

Revision: 00

Date: 01/04/2021

**NOT Gate**

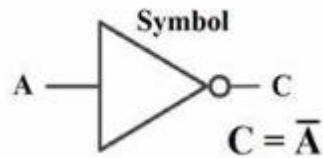

Truth Table	
INPUT	OUTPUT
A	NOT A
0	1
1	0

4.	Write the Symbol, Truth table and Output Expression for following gates. 1) AND 2) Ex-OR	5	6	1
----	--	---	---	---

As Above Stated Q2 and Q3

5.	State and Explain De-Morgan's Theorem (Any One).	5	6	2
----	--	---	---	---

A	B	A+B	$\overline{A+B}$	$\bar{A}$	$\bar{B}$	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

3 Marks

DeMorgans First Law-It states that complement of sum of variables is equal to product of its self compliments. 1 Mark

$$\overline{A+B} = \bar{A} \cdot \bar{B} \quad 1 \text{ Mark}$$

A	B	$\bar{A}$	$\bar{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

3 Marks

DeMorgans Second Law-It states that the complement of the product of variables is



**ZEAL EDUCATION SOCIETY'S  
ZEAL COLLEGE OF ENGINEERING AND RESEARCH  
NARHE | PUNE -41 | INDIA**



Record No.: **ZCOER-ACAD/R/16M**

Revision: **00**

Date: **01/04/2021**

equal to sum of its self compliments.

1 Mark

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

1 Mark

6.

Draw NOT, AND, OR Gate using NAND Gate.

5

6

3


NOT Logic



AND Logic



OR Logic

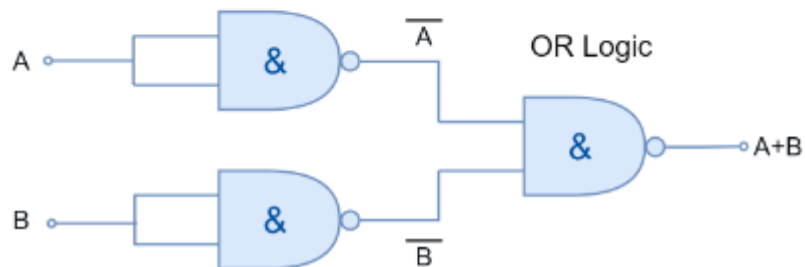

1+2+2 Marks

Course Faculty

Prof. Karuna Mahajan



**ZEAL EDUCATION SOCIETY'S**  
**ZEAL COLLEGE OF ENGINEERING AND RESEARCH**  
**NARHE | PUNE -41 | INDIA**



Record No.: ZCOER-ACAD/R/16M

Revision: 00


Date: 01/04/2021

7. Draw NOT, AND, OR Gate using NOR Gate.

5

6

2

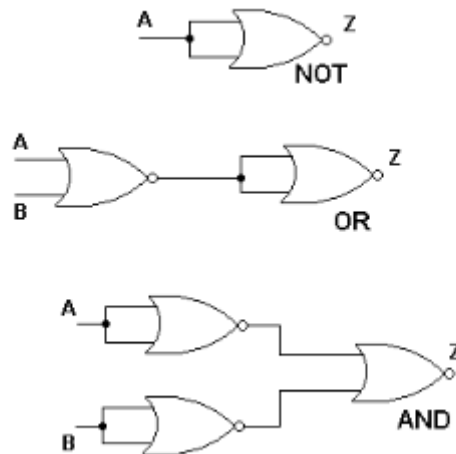

1+2+2 Marks

8. Perform the following conversions:  
a)  $(10011)_2 = (\quad)_{10}$   
b)  $(27)_{10} = (\quad)_2$

5

6

3

**1 0 0 1 1**

$$\begin{aligned}
 &1 \times 2^0 = 1 \times 1 = 1 \\
 &1 \times 2^1 = 1 \times 2 = 2 \\
 &0 \times 2^2 = 0 \times 4 = 0 \\
 &0 \times 2^3 = 0 \times 8 = 0 \\
 &1 \times 2^4 = 1 \times 16 = 16 \\
 &\text{SUM} = 19
 \end{aligned}$$

2.5 Marks

Ans: Decimal No= 19

**$(27)_{10} = (11011)_2$**

2	27	Remainder
2	13	1
2	6	1
2	3	0
2	1	1
	0	1



**ZEAL EDUCATION SOCIETY'S**  
**ZEAL COLLEGE OF ENGINEERING AND RESEARCH**  
**NARHE | PUNE -41 | INDIA**



Record No.: **ZCOER-ACAD/R/16M**

Revision: **00**

Date: **01/04/2021**

2.5 Marks

9.

Prepare the truth table for following equation in standard SOP form.

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

5

6

3

Inputs			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Inputs- 3 Marks

Output-2 Marks

10.

Minimize the Three variable logic function using K-map.

$$f(A,B,C) = \sum m(3,5,6,7)$$

5

6

3

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	0	0	1	0
A	0	1	1	1

Ans  $Y = BC + AC + AB$

Course Faculty

Prof. Karuna Mahajan



**ZEAL EDUCATION SOCIETY'S**  
**ZEAL COLLEGE OF ENGINEERING AND RESEARCH**  
**NARHE | PUNE -41 | INDIA**



Record No.: **ZCOER-ACAD/R/16M**

Revision: **00**

Date: **01/04/2021**

<p style="text-align: center;">K-Map- 2 Marks          Grouping -1 Mark          Output Y Expression-2 Marks</p>				
11.	Perform the following Binary Addition a) 1101 and 0110 b) 1111 and 0101	5	6	2
1101+0110 = 10011      2.5 marks 1111+0101=10100      2.5 marks				
12.	Perform the following Binary Subtraction a) 1100 and 0010 b) 1011 and 0111	5	6	3
1100-0010=1010      2.5 marks 1011-0111=0100      2.5 marks				
13.	Perform the following Binary Multiplication 1011 and 0101	5	6	3
<div style="text-align: center;"> <math display="block">  \begin{array}{r}  1011 \\  \times 101 \\  \hline  1011 \\  0000 \\  + 1011 \\  \hline  110111  \end{array}  </math> </div> <p>1 mark each Ans step=3 Marks            Last Ans =2 Marks</p>				